

Dieter's Nixie Tube Data Archive

This file is a part of Dieter's Nixie- and display tubes data archive

If you have more datasheets, articles, books, pictures or other information about Nixie tubes or other display devices please let me know.

Thank you!

Document in this file	Magazine "Radio-Electronics" Aug. 1969 – Article about the Elfin MG-19 readout tube
Display devices in this document	MG-19

Boost car gage accuracy in 20 minutes

60¢ ■ AUG. 1969

Radio-Electronics[®]

In These Headphones -
FM Stereo Receiver

(see page 43)


BUILD—
0-200 MHz
frequency
counter
with IC's

PROGRAMMED—
How to use
triggered
scopes

EXPERIMENT—
Digital readouts
how they work



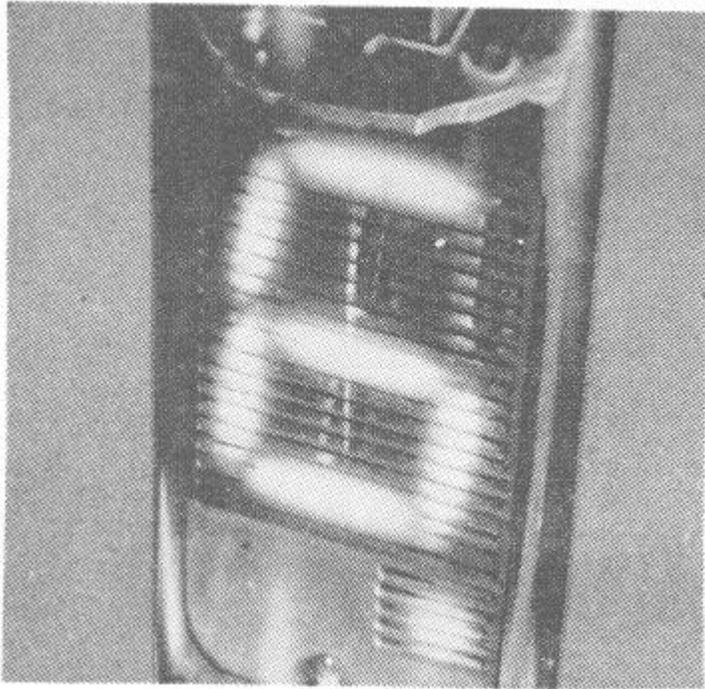RETAILER: SEE PAGE 88 FOR
SPECIAL DISCOUNT ALLOWANCE PLAN



EXPERIMENT WITH DIGITAL READOUTS

New miniature indicator lamp displays both letters and numbers. Circuits show you how to get crisp, brilliant alphanumeric readouts.

By **JIM ASHE**

The race continues, both solid-state and neon-glow alphanumeric indicators have their special advantages, but now the neons are coming on strongly in the form of some new subminiature indicators.

Alco Electronic Products Inc. (Lawrence, Mass.) recently introduced MG-19 Elfin indicators for small instrument work. Their crisp, bright red-orange images are adequate in almost any illumination.

How Elfins work

The new indicators are tiny but complex cold-cathode neon lamps. Unlike other similar devices, they offer a single-plane display composed of nine segments (Fig. 1).

Depending on your needs, a fairly complex circuit may be required to decode a binary-coded decimal or other signal. But Elfin indicators can display many alphabetic as well as all numeric characters.

Each Elfin indicator bulb has 10 electrical connections (Fig.2). Lead A is the common anode, and the other nine leads go to the

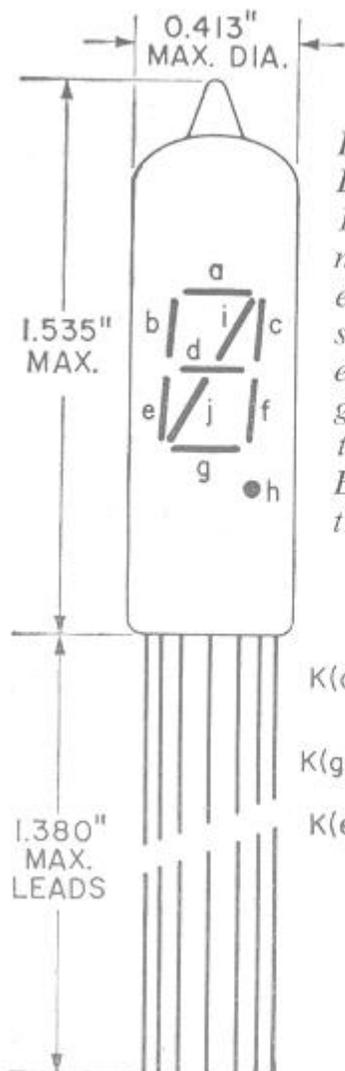


Fig. 1 (left)—Size of Elfin is just over 1½ inch. Each of the nine separate cathode elements are on the same plane. Dark elements make neon glow stand out (photo). Fig. 2 (below)—Base connections for the new indicators.

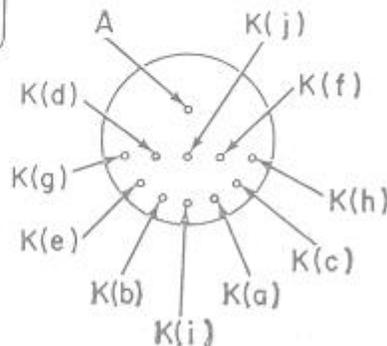


TABLE I
ELFIN SPECIFICATIONS

<u>ANODE SUPPLY:</u> 230V dc
<u>BREAKDOWN:</u> +180V dc
<u>CATHODE CURRENT:</u>
SEGMENT—500 μ A
DECIMAL PT.—200 μ A
<u>AMBIENT TEMP:</u> -65°C — +70°C
<u>DC PEAK CATHODE CURRENT:</u>
SEGMENT — 4 MA.
DECIMAL PT.—200 μ A.
<u>PULSED OPERATION PERMISSIBLE</u>

segments show in Fig. 1. If the anode is connected to about -200 volts and the cathode leads are grounded through a 220,000-ohm resistor, the segments will glow. The decimal point, a smaller element, requires a series resistor several times larger.

Electrically, the Elfin is merely a glorified neon lamp. However, its turn-on and turn-off voltages are considerably higher than ordinary neon lamps, perhaps as a result of a special gas mix for its "prolonged life span" specification. The manufacturer's specs appear in table 1. Notice the lower current for the decimal point.

The brightness of these little indicators is quite surprising. This is partly due to the light-absorbent quality of the electrical elements, which provides a dark background area even when the Elfin is unmounted. But the neon

glow is very bright in itself. Manufacturer's specs suggest 1 mA cathode current is not excessive, and tests at the level gave a brightness suitable for any ambient lighting short of direct sunlight. For longer life, the Elfins operate at several tens of microamps per cathode, but brightness is considerably reduced.

The operating curve I ran (Fig. 3) is provisional, since specified operating voltages are higher than those I obtained by testing preproduction samples I used.

This graph shows what we expect: for a given current there's a definite voltage across the map, and the voltage increases as the current rises in the usual operating range. Since neon lamps show a very sharp current-voltage dependence, we get this curve by varying the overall voltage through a large series resistor. I adjusted the current to 0.5, 1.0, and 1.5 mA, measured the voltage across the elements at each setting and checked at 0.2 mA for the decimal point. There was some variation between elements and from one tube to another.

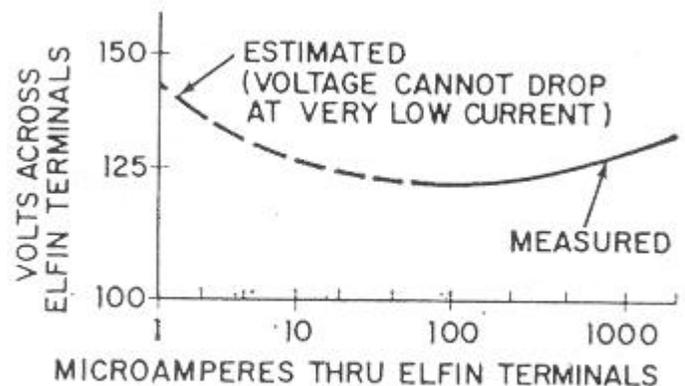


Fig. 3—Voltage-current characteristics measured from three preproduction Elfins.

Some basic circuits

Although Elfin firing and operating voltages look like something from a history book, it's not hard to generate adequate voltages at the required low currents. A gas regulator tube or two can provide stabilization. Since a voltage-regulator tube can handle up to 25 or 30 mA of output current, we can easily operate at least six Elfin at fairly high current levels.

Elfins are excellent for nearby or remote indication of switch position, servo function and other jobs where the control system consists of a switch assembly, a power supply and perhaps a lot of wire. With the diagram in Fig. 4 you can work out your own design for this purpose.

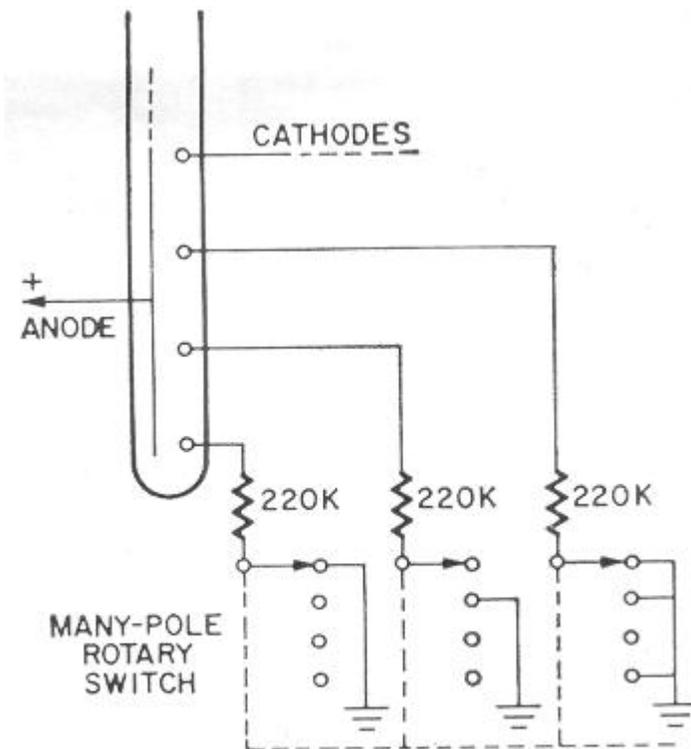


Fig. 4—Driving the Elfin from a multiple-wafer switch, at one wafer for each cathode.

Here, each Elfin cathode element has a series current-limiting resistor, with the dot element (if used) having a larger resistor since it requires less current. A single resistor is not used in the anode element, as with Nixie tubes, because as different configurations of lighted elements are selected the total anode current varies. This simple switching system requires no diodes or other semiconductors. Simply wire the fixed contacts so all the appropriate elements are connected to ground for each switch position.

In this arrangement a separate switch wafer for each element is necessary. That works out to a seven- or nine-wafer switch, and one position per character to be displayed. With diodes this complexity can be reduced to a single-wafer switch (see Fig. 5).

In position 1, only cathode K_a sees an electrical connection to ground. In position 2, only cathode K_b fires, in position 3 they both fire, and so on. Design this system to your specs by choosing a given switch position and

marking each intersection for the input line to the appropriate cathode. During assembly, wire a diode around each marked intersection.

If you don't understand what the diodes do, imagine one replaced by a piece of wire, and then run the switch through its positions. This is simply a diode matrix, requiring 49 diodes to read out the integers 0-9 from a single-pole 10-position switch.

Power diodes rated at 200 PIV can be used in the matrix rather than the more expensive signal diodes.

How about Elfin indicator control with solid-state switches? Nixies are sometimes controlled directly by the circuit shown in Fig. 6, but transistors for this application would need 200 volt V_{CEO} ratings. A catalog disclosed no possibilities of the small-signal, inexpensive variety. We will have to try strategy, and the answer appears back in Fig. 3, the measured EI curve.

By switching the Elfin between some off state of insufficient voltage to some on state of adequate current, the voltage swing can be low enough to be handled by ordinary transistors. A workable scheme appears in Fig. 7.

Fig. 5—Diode matrix arrangement permits use of single-pole switch to light tubes.


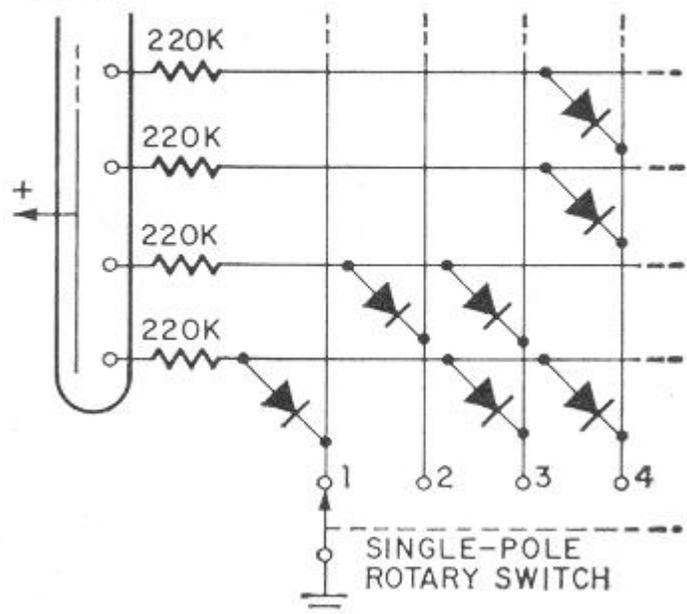


Fig. 6 (below, left)—Transistor switching arrangement possible with low-voltage Nixie tubes. Fig. 7 (below, right)—Firing voltage and typical setup to operate Elfins.

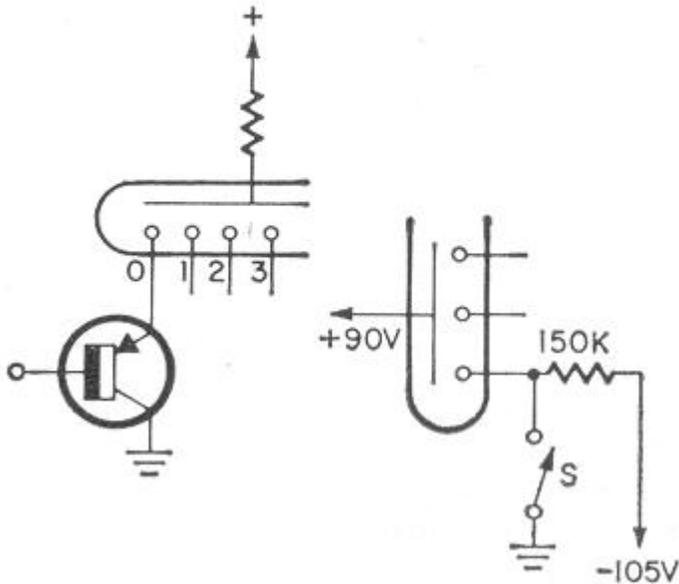

It works this way. Suppose switch *S* is closed. We have +90 volts from supply to ground through the switch. (If you feel uncomfortable about that, you're thinking about ordinary neon indicators that would be destroyed in this circuit.) Our measured EI characteristic shows there's no current flow with 90 volts applied. There will be about 0.8 mA flowing from ground to the minus supply. Then switch *S* is opened.

This gives us the sum of the positive and negative supply voltages applied to the Elfin indicator through a 150,000-ohm resistor. The Elfin fires, and the supply voltage goes to about 120 volts across the indicator, about 80 volts across the resistor, and perhaps 0.5 mA flowing. The upper switch contact falls from zero volts to -30 volts, acceptable to an ordinary transistor. We see this requires a pnp transistor.

Now let's do this with transistors. The complete indicator circuit appears in Fig. 8. Here, a bias resistor from base to minus holds each pnp transistor saturated until a turnoff signal is applied. This signal switches the transistor off, and its Elfin element lights up. Diodes D1, etc. prevent excessive transistor-base turnoff voltages, and may be omitted in many designs of known drive and transistor ratings.

This circuit is controlled by positive logic, and since the transistor base terminals are clamped only a few hundred millivolts negative, we can easily use conventional positive-supply, positive-logic ICs. Now, if you want to drive the indicator from a parallel line at one lead per character, you can use the matrix idea previously mentioned to translate from character logic to element logic.

There are now lots of appropriate transistors. Since the V_{CE0} rating is a pessimistic one established under open-base connections, a 25-volt rating may be adequate. I'd choose at least 30 volts, and General Electric's 2N5365 transistor, priced at 55 cents, is rated at V_{CE0} -40 volts.

Fig. 9 shows a simple power supply circuit. If later samples of the Elfins turn out to have

Fig. 8 (below)—Transistor circuit for controlling Elfins. High V_{CE} is not needed, since transistors are clamped.


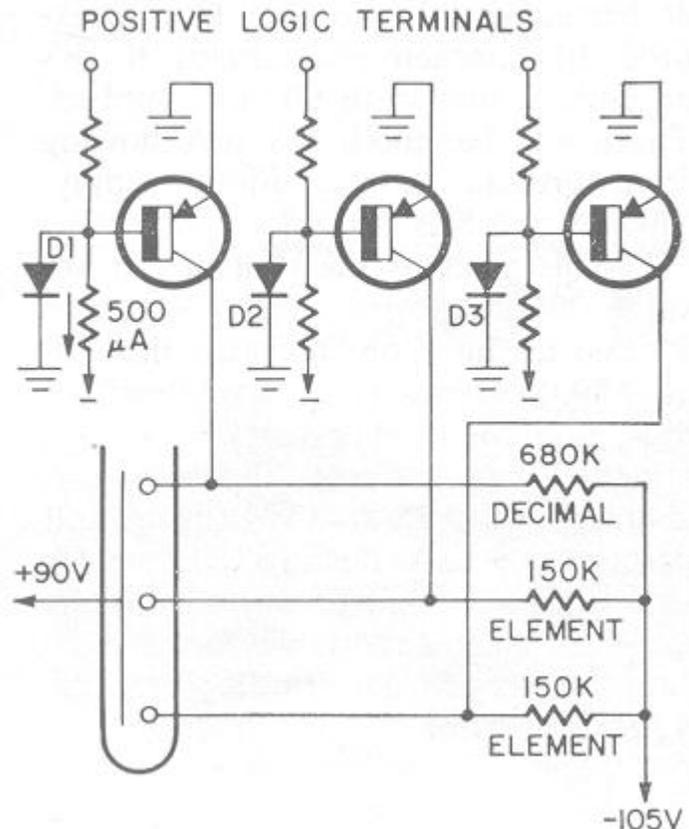


Fig. 9 (below)—Power supply for indicators can use extra VR tube for safety.

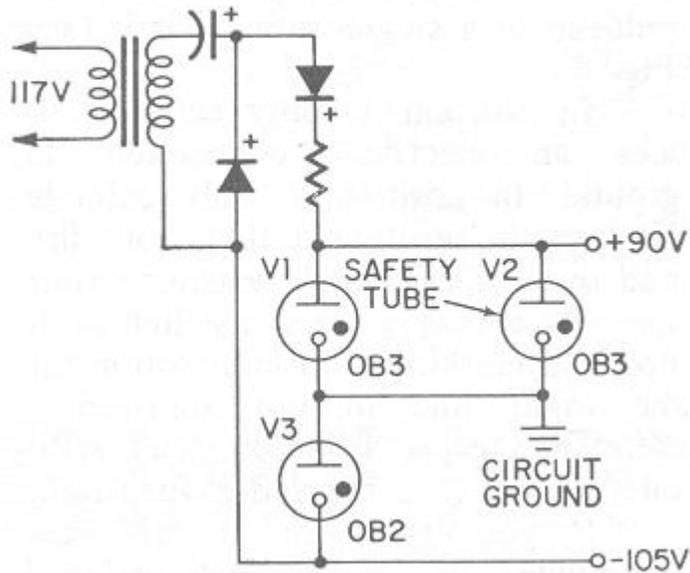

higher operating voltages than my preproduction samples, simply choose higher-voltage regulator tubes and review the design.

What if regulator V1 fails? That would overvolt the Elfin's in turnoff, and we could expect a disastrous failure costing us an Elfin and many transistors per integer displayed. The answer is simple: simply add another similar tube in parallel with V1 and mark on the chassis which tube should fire in normal operation. If you check one day and the wrong tube is lit, your safety factor has diminished but is easily restored by a new VR tube.